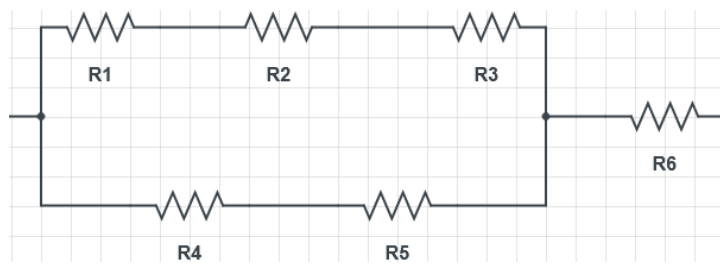


1. Berechne alle fehlenden Werte!

Spannung		Stromstärke		Widerstand	
U_G	220 V	I_G	A	R_G	Ω
U_1	V	I_1	A	R_1	15 Ω
U_2	V	I_2	A	R_2	25 Ω
U_3	V	I_3	A	R_3	40 Ω
U_4	V	I_4	A	R_4	35 Ω
U_5	V	I_5	A	R_5	45 Ω
U_6	V	I_6	A	R_6	160 Ω



Übung

Grundlagen Elektro

Name: